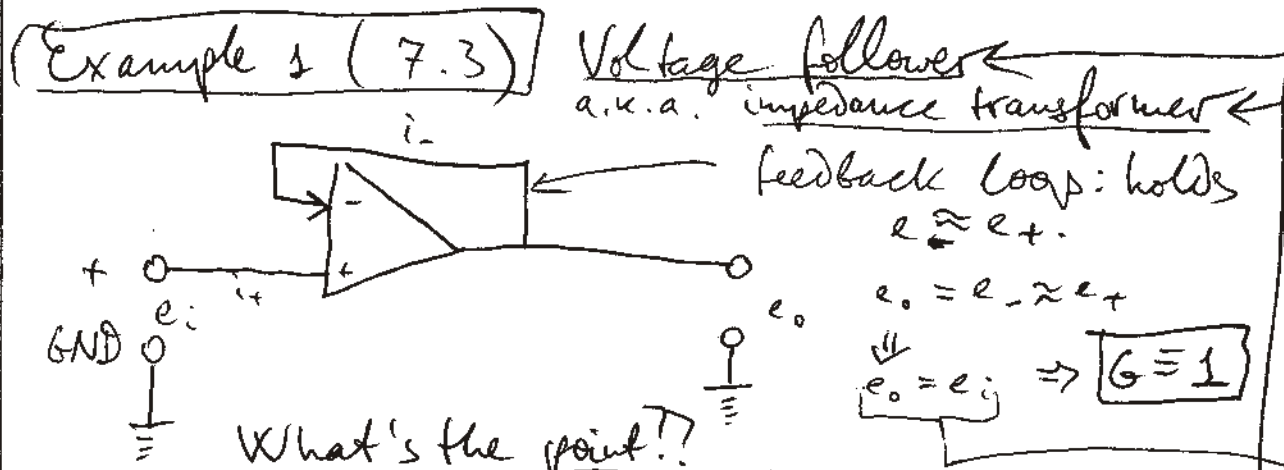


Op-Amp Applications.

NB: terminals not used are not shown.

Exclusion: power-supply inputs
(always used, never shown)

Negative feedback loop: necessary because of likelihood of saturation. Circuits w/o feedback loop - almost never used.



$i_+ \sim 10^{-12} \div 10^{-9} \text{ A}$ (our input impedance is large)


Output current $\sim 25 \text{ mA}$ (greatly amplified)

Input impedance $\sim 10^{12} \Omega$

Output impedance $< 1 \Omega$.

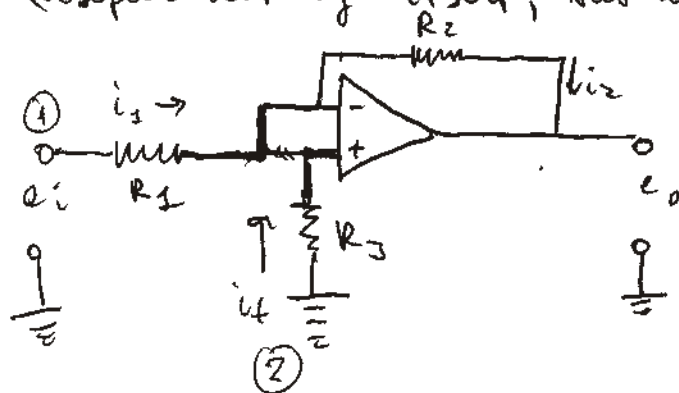Example 2 (7.4) Inverting amplifier

(useful not by itself, but as a part of a circuit).



R_2 - feedback resistor.

Resistance betw. ① and ②
 $\sim 10^{12} \Omega$ (op. amp. input impedance).

$\Downarrow$
 $i_+ \approx 0$.

Kirchoff rule for i_1, i_2, i_+ : $i_+ = 0 \Rightarrow i_1 = i_2$.

$$\frac{e_i - 0}{R_1} = i_1 ; \quad \frac{0 - e_o}{R_2} = i_2 \quad \frac{e_i}{R_1} = -\frac{e_o}{R_2}$$


Phase inverted! $\boxed{e_o = -\frac{R_2}{R_1} e_i}$ $G = -\frac{R_2}{R_1}$

Usually R_3 is set @ $R_3 = \frac{R_1 R_2}{R_1 + R_2}$

to make input impedances @ $\ominus$ and $\oplus$ terminals of op amp equal.

Example 3 (7.5)

Noninverting amplifier

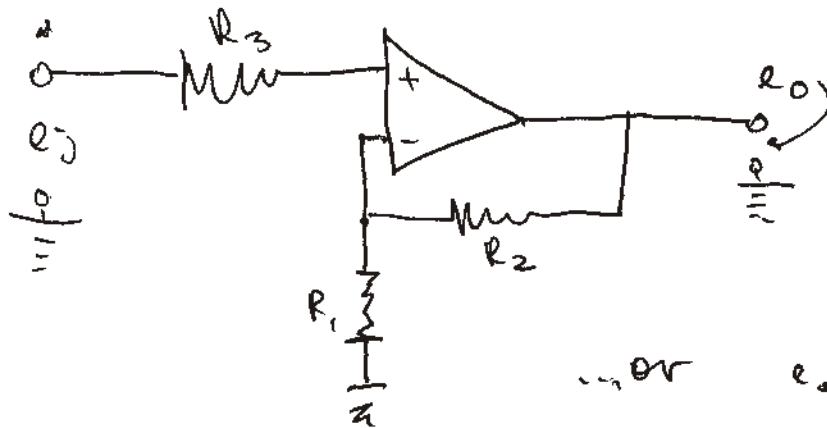

$$e_+ = e_i$$

$$e_- = e_+ \text{ (negative feedback is present)}$$

$$e_- = \frac{R_1}{R_1 + R_2} e_o$$


$$\text{... or } e_o = \frac{R_1 + R_2}{R_1} e_i$$

$$G = \frac{R_1 + R_2}{R_1}$$

R_3 - choose as in prev. example

Example 4 (7.6)

Differential amplifier

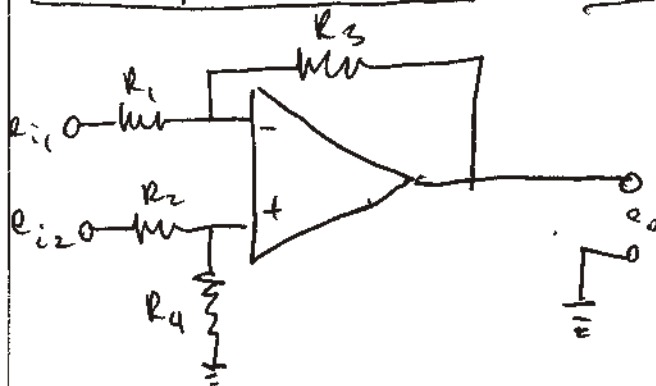

$$\text{Set } R_1 = R_2$$

$$R_3 = R_4$$

Somewhat similar to inverting amp., but uses $e_{i1} - e_{i2}$ inst. of $e_i - 0$.

$$e_o = \frac{R_3}{R_1} (e_{i1} - e_{i2})$$



Some caveats: need accurate resistor matching to get high CMRR

* can minimize offset with adjustment by making input resistances @ - and + equal.

Voltage comparator

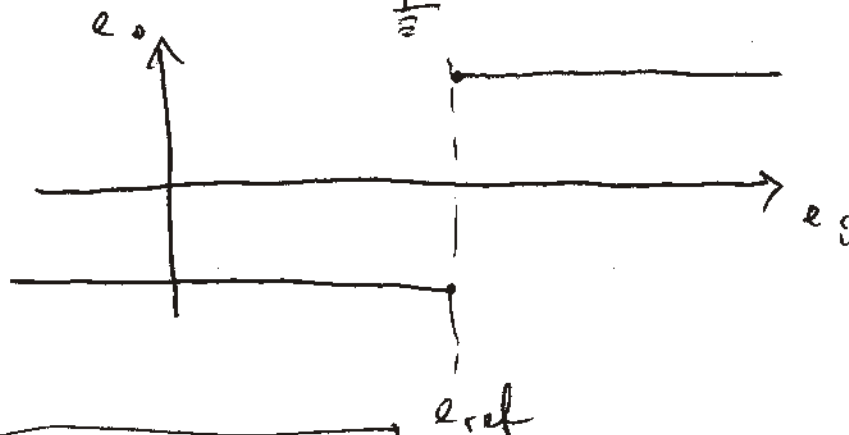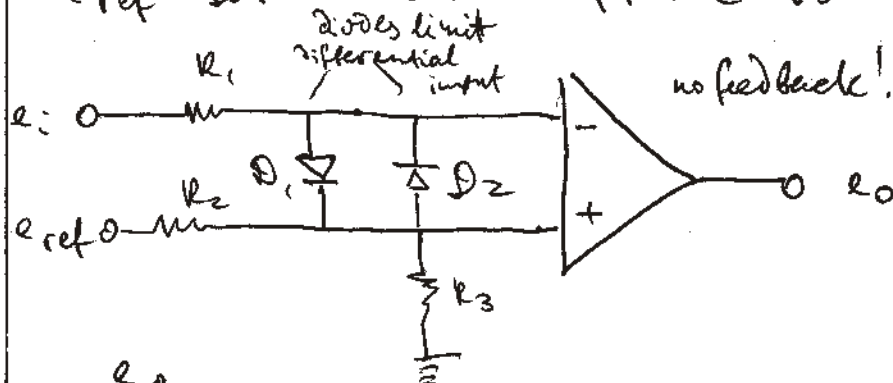Example 5 (7.8)

e_{ref} - set to desired reference voltage.



1) $e_i > e_{ref}$:
output positively saturated


2) $e_i < e_{ref}$:
output negatively saturated

$$R_3 \approx \frac{R_2 R_3}{R_2 + R_3}$$

(to equalize @ and ⊕ impedances)

Example 6 (7.9)

Summing amplifier

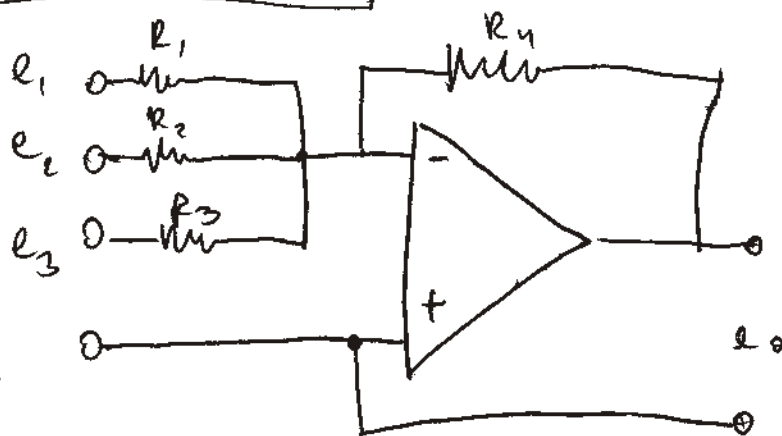

$$e_o = - \left(e_1 \frac{R_4}{R_1} + e_2 \frac{R_4}{R_2} + e_3 \frac{R_4}{R_3} \right)$$

$$R_1 = R_2 = R_3 = R \Rightarrow$$

$$e_o = - \frac{R_4}{R} (e_1 + e_2 + e_3)$$

spin-off of inverting amp.